

High-frequency Power Electronics with eGaN Devices



Jungwon Choi, ECE department



UNIVERSITY *of* WASHINGTON





Plasma Generation

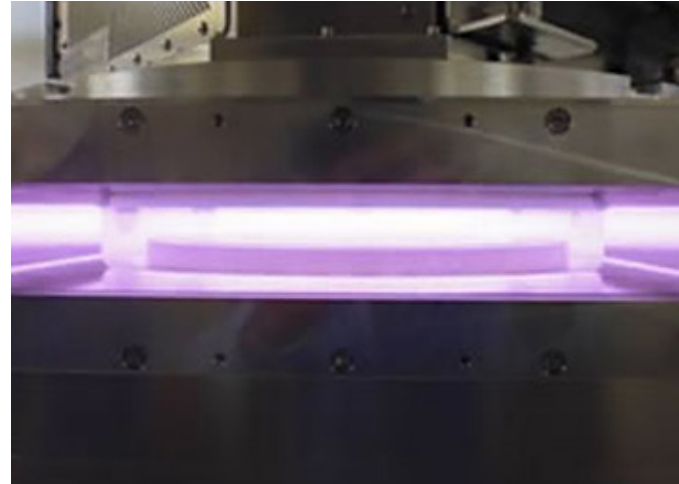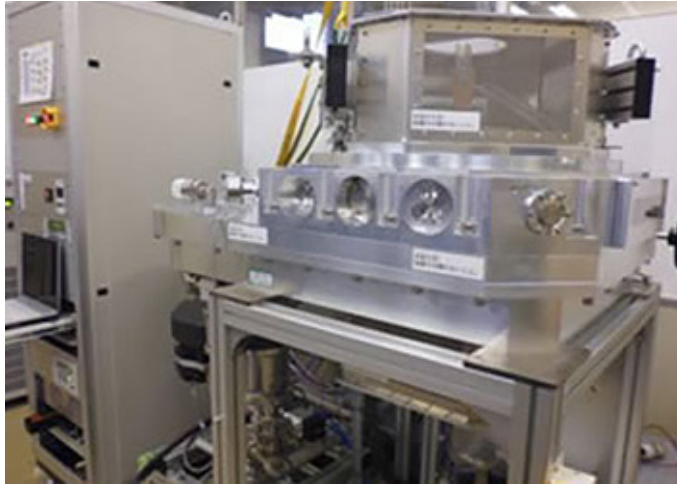

- ❑ Radio-frequency (RF) power amplifiers (PA) are used in plasma generation processes
 - High (3-30 MHz) or very high (30-300 MHz) frequency ranges
 - Over 1 kW output power
- ❑ Need to provide constant output power with load variations (resistive, inductive or capacitive).

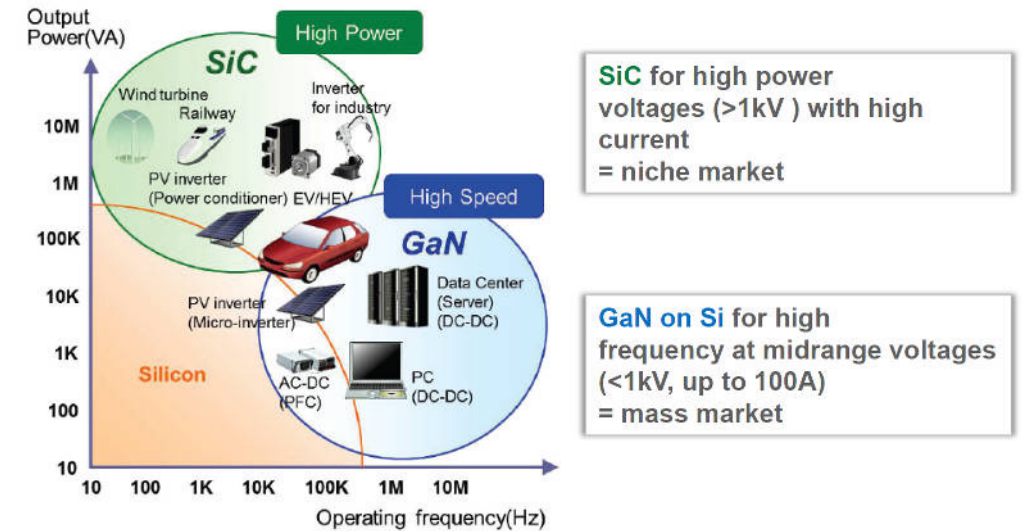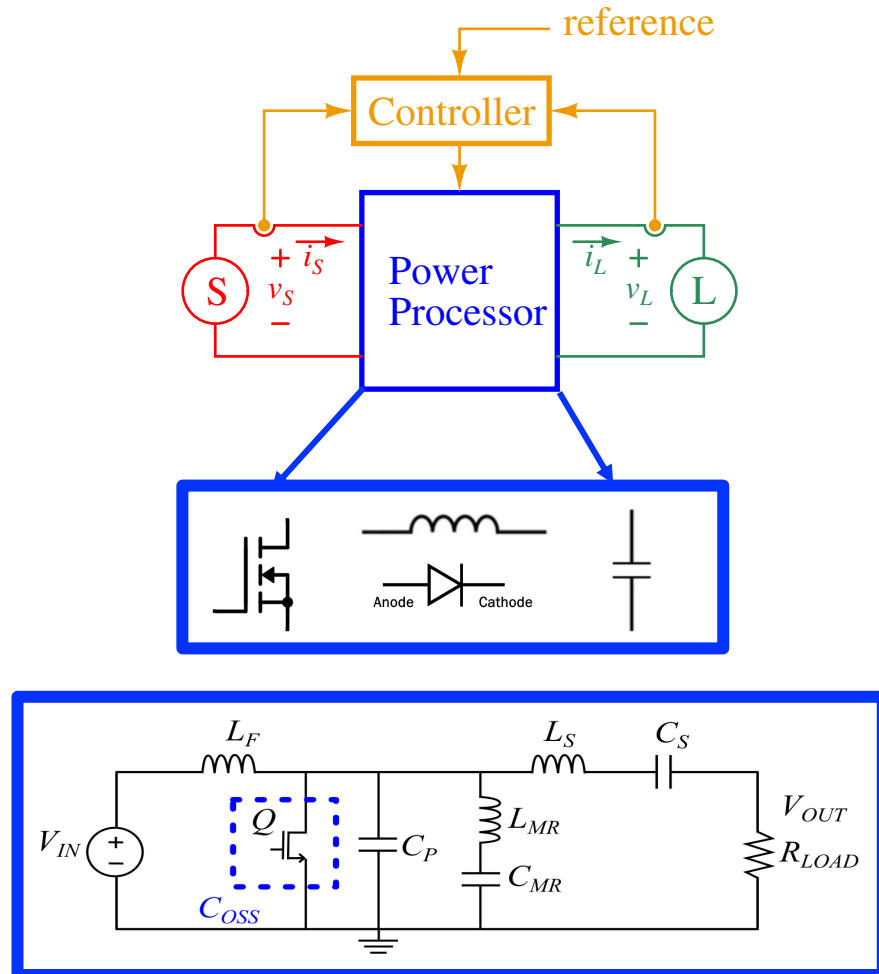Resonant Converter with Wide Bandgap Devices







Challenges


- ❑ Limited by its uniquely small packaging and structure in high-frequency, high-power applications.
- ❑ Switching losses in eGaN Devices.

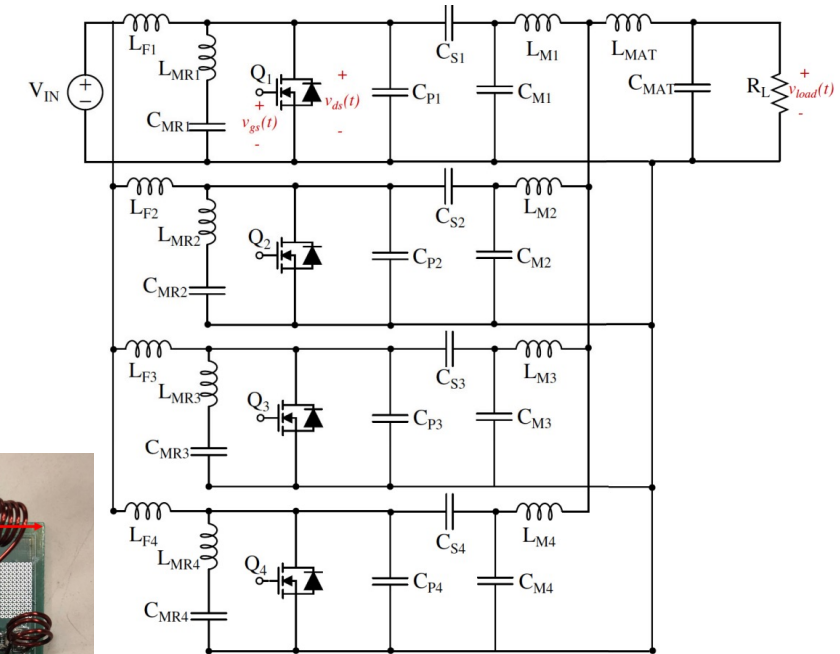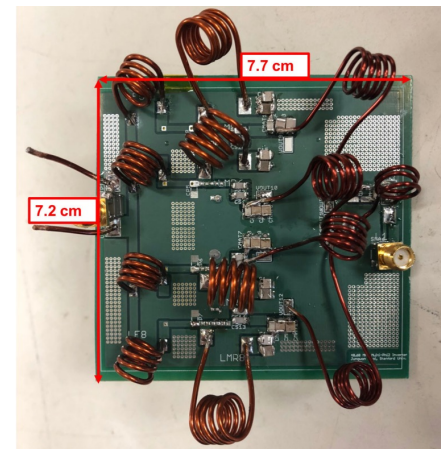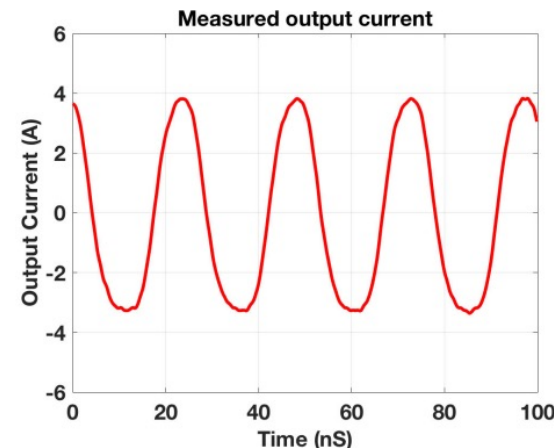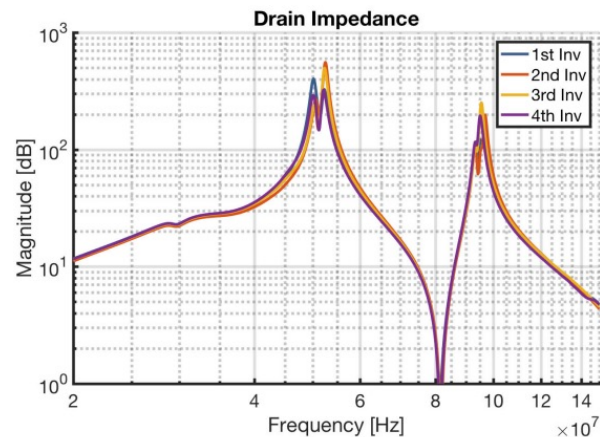40.68 MHz, 1.2 kW Power Combining Resonant Inverter

- Four eGaN FETS (GS66506T) with four gate drivers (ISL55110).
- 195 V of input voltage, 1174 W of output voltage with 83% of efficiency (higher than conventional linear amplifier).



GaN Devices in Resonant Inverter

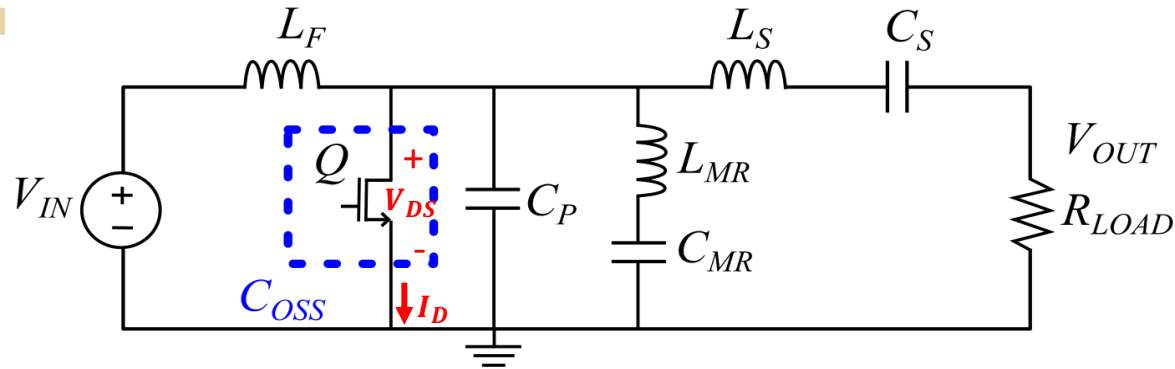

□ However, the GaN device is limited by its uniquely small packaging and structure in high power applications (**>1kW**).

High-power + high-frequency operation



Higher device losses

Assuming ZVS is achieved in the resonant inverter, the switching losses mainly consist of


- Losses due to $R_{DS,ON}$
- Losses due to turn-off transition
- Losses due to charging and discharging of device output capacitance, C_{OSS}

Solution






Parallel GaN Devices to reduce conduction loss, increase power capability and increase device reliability.

Optimum Number of Parallel Devices

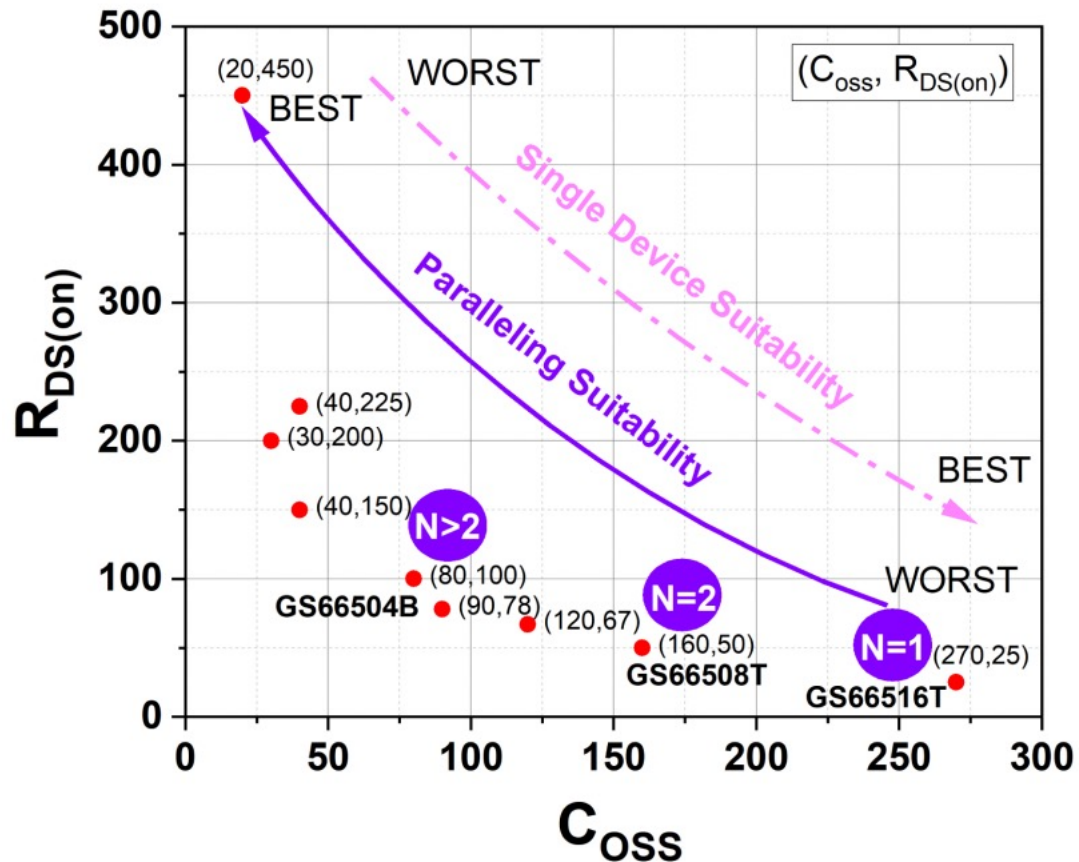


Device	Parameter	One	Two	Three	Four
GS66504B	C_P [pF]	430	350	280	200
	(Total) P_{Device_Loss} [W]	7.3	4.4	3.6	3.6
	P_{OUT} [W]	920	970	980	1000
	η [%]	95.8	96.4	96.4	96.3
GS66508T	C_P [pF]	330	180	0	—
	(Total) P_{Device_Loss} [W]	5.1	3.8	4.2	—
	P_{OUT} [W]	970	1000	1100	—
	η [%]	96.3	96.2	96.0	—

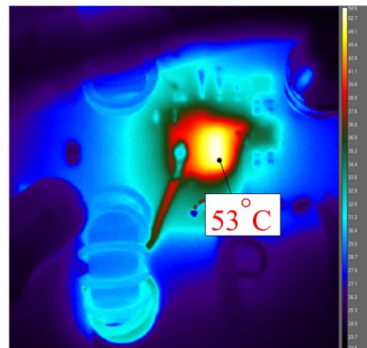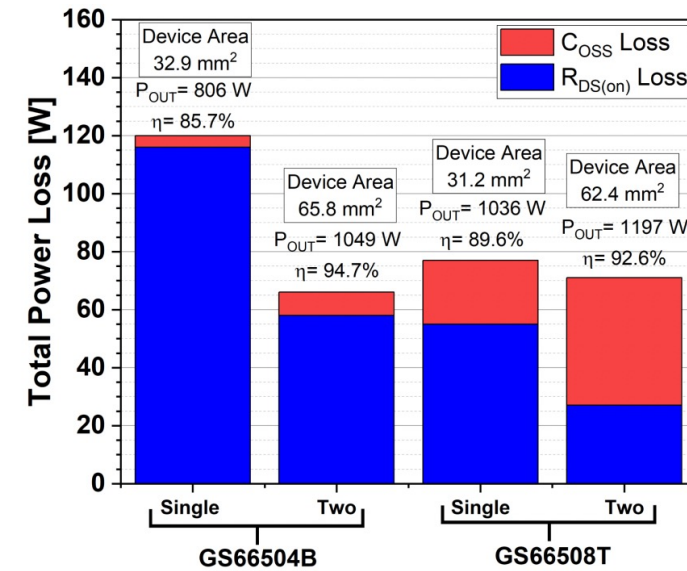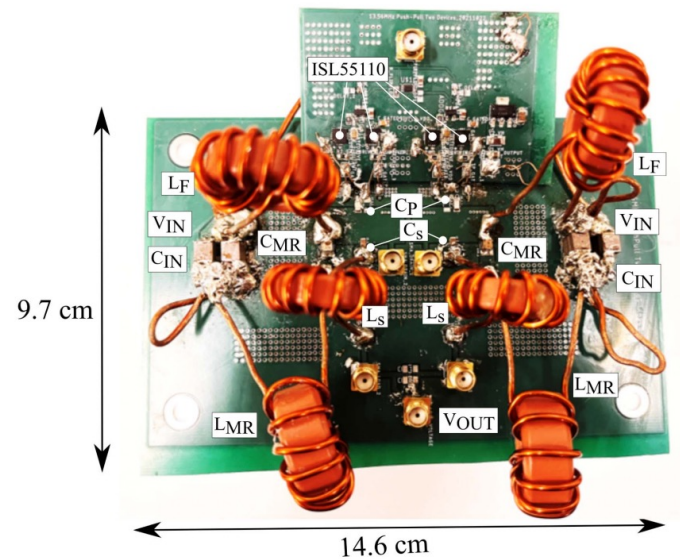
Prototype of Resonant Inverter with Multiple Devices




(a)

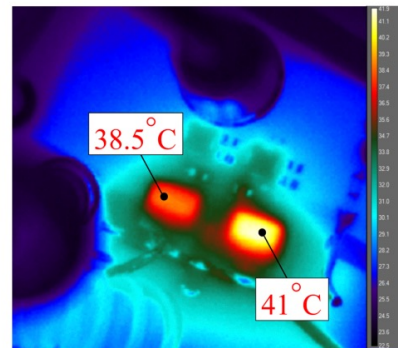

(b)

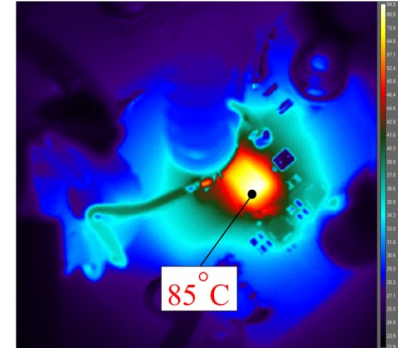

(c)

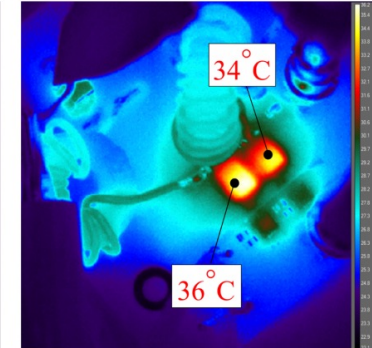

(d)

Thank you!